

- In an n-type silicon, which of the following statement is true:
 - Electrons are majority carriers and trivalent atoms are the dopants.
 - Electrons are minority carriers and pentavalent atoms are the dopants.
 - Holes are minority carriers and pentavalent atoms are the dopants.
 - Holes are majority carriers and trivalent atoms are the dopants.
- Which of the statements given in Exercise 14.1 is true for p-type semiconductors?
- Carbon, silicon and germanium have four valence electrons each. These are characterized by valence and condition bands separated by energy band gap respectively equal to $(E_g)_C$, $(E_g)_{Si}$ and $(E_g)_{Ge}$. Which of the following statements is true?
 - $(E_g)_{Si} < (E_g)_{Ge} < (E_g)_C$
 - $(E_g)_C < (E_g)_{Ge} > (E_g)_{Si}$
 - $(E_g)_C > (E_g)_{Si} > (E_g)_{Ge}$
 - $(E_g)_C = (E_g)_{Si} = (E_g)_{Ge}$
- In an unbiased p-n junction, holes diffuse from the p-region to n-region because
 - Free electrons in the n-region attract them.
 - They move across the junction by the potential difference.
 - Hole concentration in p-region is more as compared to n-region.
 - All the above
- When a forward bias is applied to a p-n junction, it
 - Raises the potential barrier.
 - Reduces the majority carrier current to zero.
 - Lowers the potential barrier.
 - None of the above.
- For transistor action, which of the following statements are correct:
 - Base, emitter and collector regions should have similar size and doping concentrations.
 - The base region must be very thin and lightly doped.
 - The emitter junction is forward biased and collector junction is reverse biased.
 - Both the emitter junction as well as the collector junction are forward biased.
- For a transistor amplifier, the voltage gain
 - remains constant for all frequencies.
 - is high at high and low frequencies and constant in the middle frequency range.
 - is low at high and low frequencies and constant at mid frequencies.
 - None of the above.
- In half-wave rectification, what is the output frequency if the input frequency is 50 Hz. What is the output frequency of a full-wave rectifier for the same input frequency.
- For a CE-transistor amplifier, the audio signal voltage across the collected resistance of 2 k Ω is 2 V. suppose the current amplification factor of the transistor is 100, find the input signal voltage and base current, if the base resistance is 1 Ω .
- Two amplifiers are connected one after the other in series (cascaded). The first amplifier has a voltage gain of 10 and the second has a voltage gain of 20. If the input signal is 0.01 volt, calculate the output ac signal.